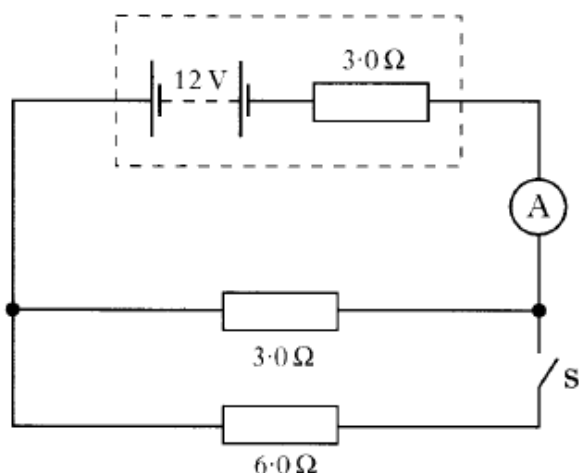


## Exercise 8 - Emf and Internal Resistance

### Past Paper Homework Questions


1. A battery of e.m.f.  $12\text{ V}$  and internal resistance  $3.0\ \Omega$  is connected in a circuit as shown.



When switch **S** is closed the ammeter reading changes from

- A  $2.0\text{ A}$  to  $1.0\text{ A}$   
 B  $2.0\text{ A}$  to  $2.4\text{ A}$   
 C  $2.0\text{ A}$  to  $10\text{ A}$   
 D  $4.0\text{ A}$  to  $1.3\text{ A}$   
 E  $4.0\text{ A}$  to  $6.0\text{ A}$ .
3. The e.m.f. of a battery is
- A the total energy supplied by the battery  
 B the voltage lost due to the internal resistance of the battery  
 C the total charge which passes through the battery  
 D the number of coulombs of charge passing through the battery per second  
 E the energy supplied to each coulomb of charge passing through the battery.

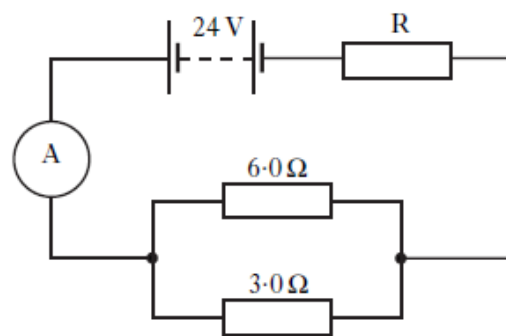
2. A battery of e.m.f.  $24\text{ V}$  and negligible internal resistance is connected as shown.



The reading on the ammeter is  $2.0\text{ A}$ .

The resistance of **R** is

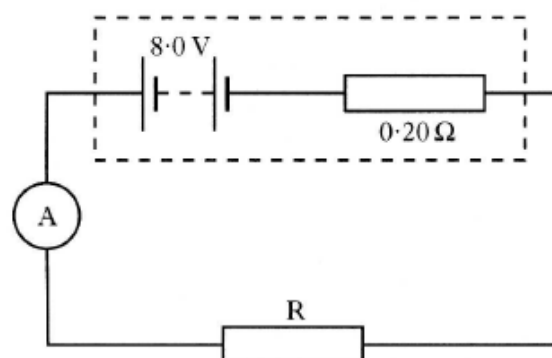- A  $3.0\ \Omega$   
 B  $4.0\ \Omega$   
 C  $10\ \Omega$   
 D  $12\ \Omega$   
 E  $18\ \Omega$ .
4. In the following circuit, the battery has an e.m.f. of  $8.0\text{ V}$  and an internal resistance of  $0.20\ \Omega$ .




The reading on the ammeter is  $4.0\text{ A}$ .

The resistance of **R** is


- A  $0.5\ \Omega$   
 B  $1.8\ \Omega$   
 C  $2.0\ \Omega$   
 D  $2.2\ \Omega$   
 E  $6.4\ \Omega$ .

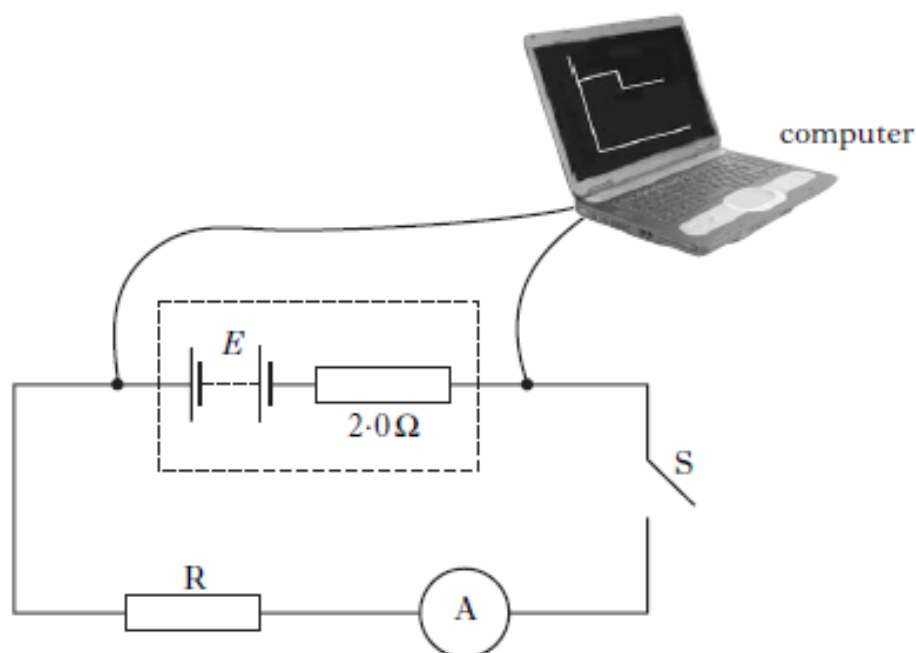5. A power supply of e.m.f.  $E$  and internal resistance  $2.0\ \Omega$  is connected as shown.




The computer connected to the apparatus displays a graph of potential difference against time.

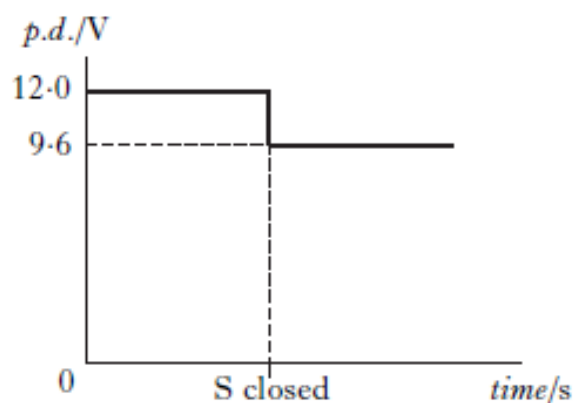The graph shows the potential difference across the terminals of the power supply for a short time before and after switch  $S$  is closed.



- (a) State the e.m.f. of the power supply. 1
- (b) Calculate:
- (i) the reading on the ammeter after switch  $S$  is closed; 2
- (ii) the resistance of resistor  $R$ . 1

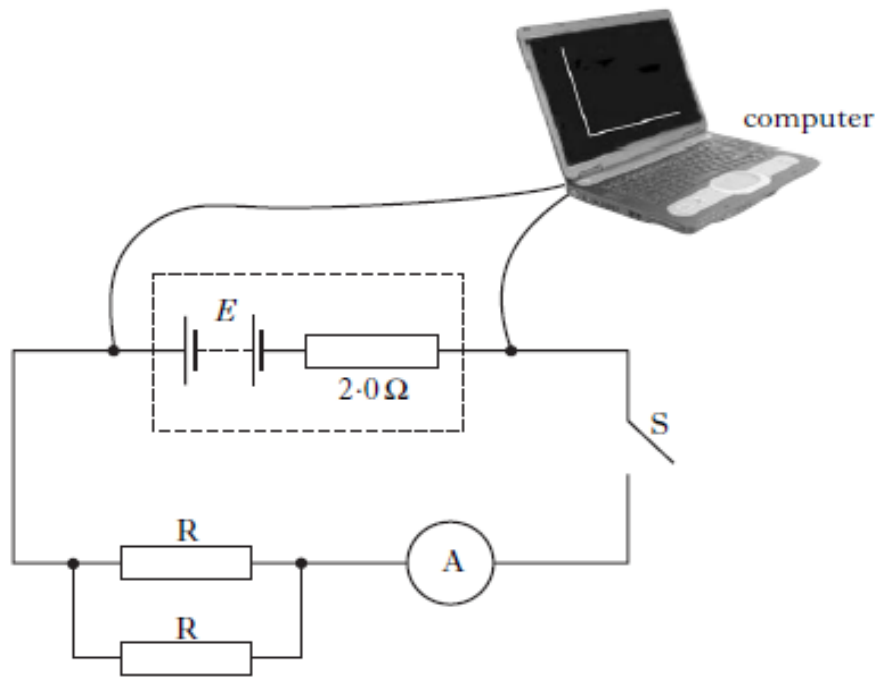- (c) Switch S is opened. A second identical resistor is now connected in parallel with R as shown.



The computer is again connected in order to display a graph of potential difference against time.




Copy and complete the new graph of potential difference against time showing the values of potential difference before and after switch S is closed.

6. Electrically heated gloves are used by skiers and climbers to provide extra warmth.



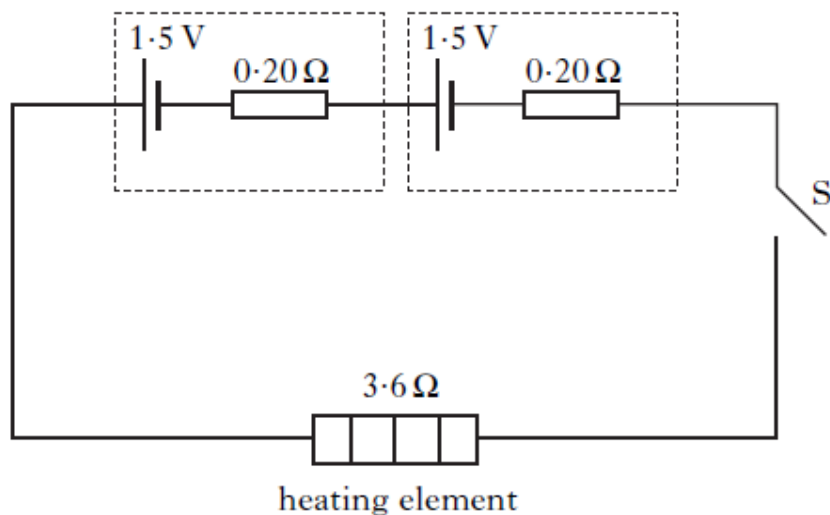- (a) Each glove has a heating element of resistance  $3.6 \Omega$ .

Two cells, each of e.m.f.  $1.5 \text{ V}$  and internal resistance  $0.20 \Omega$ , are used to operate the heating element.



Switch S is closed.

- (i) Determine the value of the total circuit resistance. 1
- (ii) Calculate the current in the heating element. 2
- (iii) Calculate the power output of the heating element. 2
- (b) When in use, the internal resistance of each cell gradually increases.  
What effect, if any, does this have on the power output of the heating element?  
Justify your answer. 2
- (7)

7. (a) A supply of e.m.f.  $10.0\text{ V}$  and internal resistance  $r$  is connected in a circuit as shown in Figure 1.

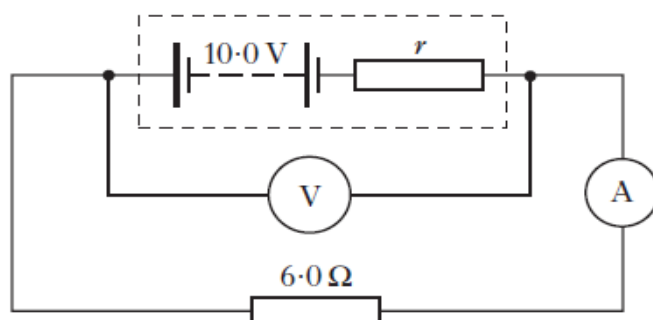


Figure 1

The meters display the following readings.

$$\text{Reading on ammeter} = 1.25\text{ A}$$

$$\text{Reading on voltmeter} = 7.50\text{ V}$$

- (i) What is meant by an *e.m.f. of  $10.0\text{ V}$* ? 1
- (ii) Show that the internal resistance,  $r$ , of the supply is  $2.0\ \Omega$ . 1
- (b) A resistor  $R$  is connected to the circuit as shown in Figure 2.

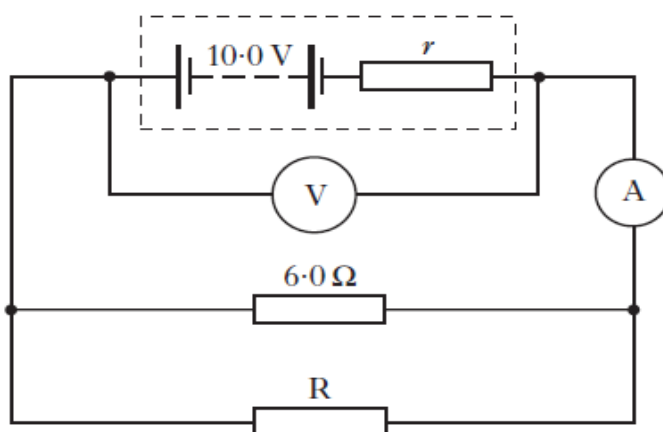


Figure 2


The meters now display the following readings.

$$\text{Reading on ammeter} = 2.0\text{ A}$$

$$\text{Reading on voltmeter} = 6.0\text{ V}$$

- (i) Explain why the reading on the voltmeter has decreased. 2
- (ii) Calculate the resistance of resistor  $R$ . 3
- (7)

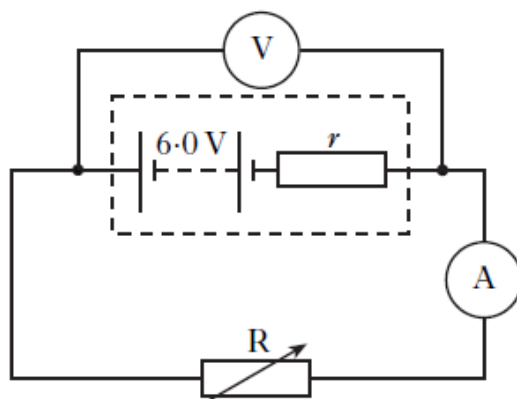
8. A battery of e.m.f.  $6.0\text{ V}$  and internal resistance,  $r$ , is connected to a variable resistor  $R$  as shown.



The graph shows how the current in the circuit changes as the resistance of  $R$  increases.

The graph shows how the current in the circuit changes as the resistance of  $R$  increases.

current/A

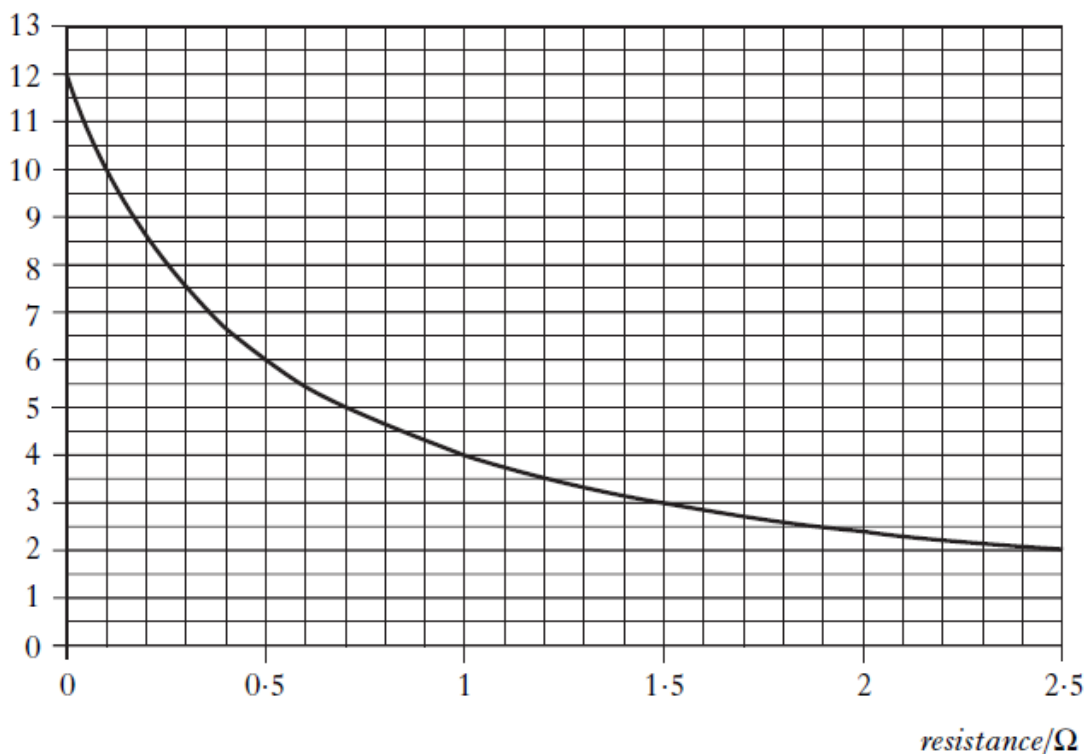

- (a) Use information from the graph to calculate:
- the lost volts in the circuit when the resistance of  $R$  is  $1.5\ \Omega$ ; 2
  - the internal resistance,  $r$ , of the battery. 2
- (b) The resistance of  $R$  is now increased.  
 What effect, if any, does this have on the lost volts?  
 You must justify your answer. 2

**30 marks**